

ASSIGNMENT-1

Max. Marks: 25

Last date of submission: 22/09/2025

Note: Answer *all* questions. Assume suitable missing data, if any.

CO1: Explain the principles of operation of semiconductor devices such as diode, BJT, JFET and MOSFET.

CO2: Apply the basic principles to solve numerical problems related to diode and transistors and their applications.

CO3: Simplify logical expressions using Boolean algebra and K-maps.

CO4: Design combinational and sequential digital circuits.

CO5: Explain the concepts of analog modulation schemes.

CO6: Describe the concepts of digital modulation schemes.

1. Determine V_o and I_D for the networks of **Fig. 1**.

[CO2] [2 marks]

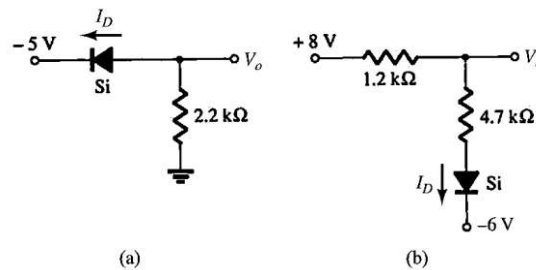


Fig.1

2. Determine v_o and the required PIV rating of each diode for the configuration of **Fig.2**. In addition, determine the maximum current through each diode.

[CO2] [3 marks]

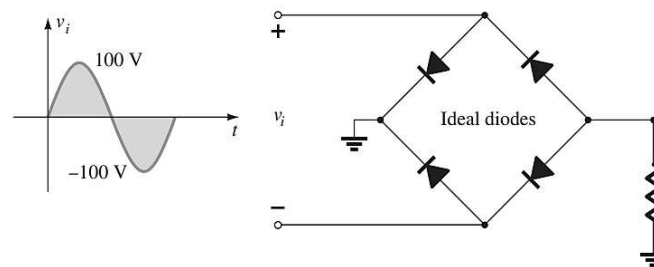


Fig.2

3. Sketch v_o for each network of **Fig. 3** for the input shown.

[CO2] [3 marks]

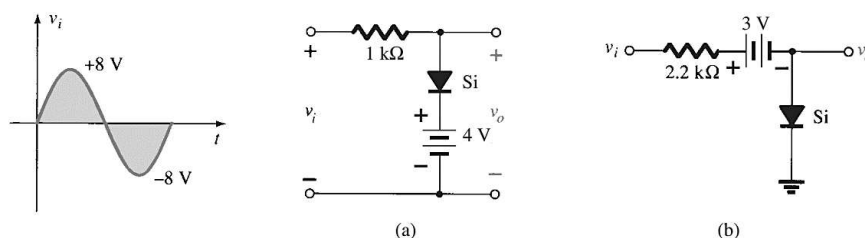


Fig.3

4. Sketch v_o for the network shown in **Fig.4**. Compare discharge time of a capacitor to half the period of the applied signal. [CO2] [3 marks]

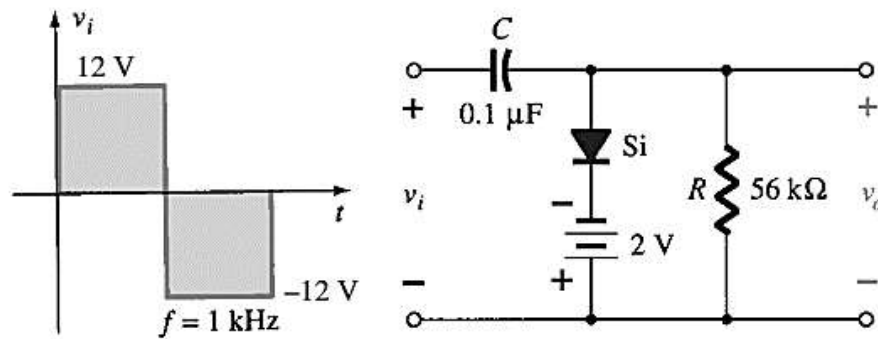


Fig.4.

5. a. Determine V_L , I_L , I_Z , and I_R for the network of **Fig. 5**, if $R_L = 180 \Omega$.
 b. Repeat part (a) if $R_L = 470 \Omega$.
 c. Determine the value of R_L that will establish maximum power conditions for the Zener diode.
 d. Determine the minimum value of R_L to keep Zener diode is in the “on” state. [CO2] [4 marks]


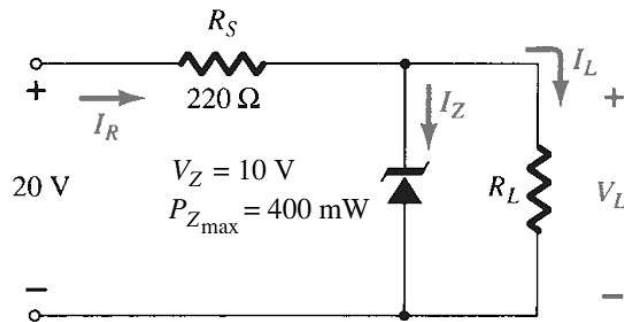


Fig.5

6. Given the information appearing in **Fig. 6**, determine:
 a. I_C
 b. V_E
 c. V_{CC}
 d. V_{CE}
 e. V_B
 f. R_1

[CO2] [3 marks]

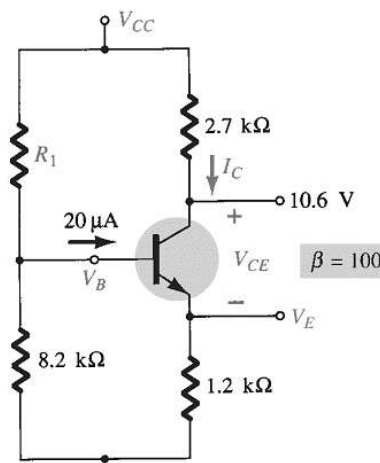

7. Derive a relationship between α , β and γ of a BJT. [CO1] [2 marks]
8. What is the significant difference between the construction of an enhancement-type MOSFET and a depletion-type MOSFET? [CO1] [2 marks]
9. a. Given $I_{DSS} = 12 \text{ mA}$ and $V_p = -4 \text{ V}$, sketch the transfer characteristics for the JFET.
b. Sketch the drain characteristics for the device of part (a). [CO2] [3 marks]

*****END*****